



For builds that do not require variable voltage solder a jumper wire across P01 terminals (R3 in schematic).
 Output voltage will be set by R2. Assuming 1% tolerance:
 R2=220 ohm => Vout = 5.91–6.02
 R2=267 ohm => Vout = 4.97–5.06
 R2=330 ohm => Vout = 4.14–4.21
 R2=430 ohm => Vout = 3.31–3.37

The Baby Potato PCB is a small backpack for, and approximately the same size as, the OKR–T6/10. It is based on /u/slumberland's Potato v2 schematics (recreated here) which is heavily influenced by designs/schematics from Mamu, The Goss, and others. Designed by a modder, for modders. Documentation is intentionally sparse. While the board itself is inherently safe, the batteries that one can attach to it are very much not. Misuse and Abuse can lead to the loss of a face. Be careful and direct questions to www.reddit.com/r/openpv

The Baby Potato is available for purchase at OshPark
http://oshpark.com/shared_projects/A80Nd2IR

Design files and Documentation are published on Github
https://github.com/rdasx/baby_potato

All Components on the Baby Potato board are 1206 (SMT) Footprint. Capacitors are MLCC type at \$0.40/ea and are optional but recommended. Don't be cheap. Resistors are thick film type and \$0.10/ea. Connect your own powersupply (12V or 2 series Li-ion cells), potentiometer (optional), momentary power switch, power connector (510), and OKR–T6/10 module.

This Project is released under the TAPR Open Hardware License.
<http://www.tapr.org/ohl>

It is free for both commercial and hobby use.
 Attribution is requested, but not a required term of license.
 I, /u/Militancy, make absolutely no profit on the sale or use of these boards.
 No support or warranty is expressed or implied.

File: potato.sch	Baby Potato		Drawn By: /u/Militancy
Sheet: /			
Title: Potato v2 Schematics, recreated from /u/slumberland 's schematics			
Size: USLetter	Date: 23 mar 2014	Rev: 0.1.a	
KiCad E.D.A.			Id: 1/1